 



Embedded 1
Lab Report #2
Justin Evron
2/6/19

PRELAB

1. $Y = ((A \text{ XOR } B) \text{ XOR } C)$
 $C_{out} = ((A \text{ XOR } B) \text{ and } C_{in}) \text{ or } A \text{ and } B$
- 2.



3.

 


Adders

Operation

The circuit should add the A and B inputs and output them to S with C_out acting as the overflow indicator.

Schematic

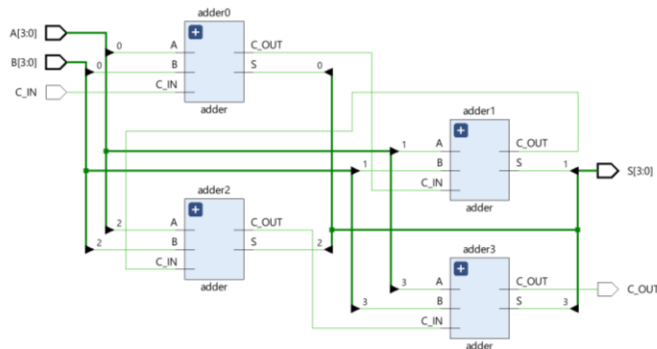

Design

1 bit adder

entity adder is

```
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      C_IN : in STD_LOGIC;  
      C_OUT : out STD_LOGIC;  
      S : out STD_LOGIC);
```

end adder;

architecture Behavioral of adder is

signal AB : STD_LOGIC;

begin

```
AB <= A XOR B;
```

```
S <= AB XOR C_IN;
```

```
C_OUT <= (AB AND C_IN) OR (A AND B);
```

end Behavioral;

Ripple Adder

entity ripple_adder is

```
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);  
      B : in STD_LOGIC_VECTOR (3 downto 0);  
      C_IN : in STD_LOGIC;  
      C_OUT : out STD_LOGIC;  
      S : out STD_LOGIC_VECTOR (3 downto 0));
```

end ripple_adder;

architecture Behavioral of ripple_adder is

component adder is

```

        Port ( A : in STD_LOGIC;
              B : in STD_LOGIC;
              C_IN : in STD_LOGIC;
              C_OUT : out STD_LOGIC;
              S : out STD_LOGIC);
    end component;
    signal C0, C1, C2 : STD_LOGIC;
begin
    adder0: adder
    port map(A => A(0),
            B => B(0),
            C_IN => C_IN,
            S => S(0),
            C_OUT => C0);
    adder1: adder
    port map(A => A(1),
            B => B(1),
            c_IN => C0,
            S => S(1),
            C_OUT => C1);
    adder2: adder
    port map(A => A(2),
            B => B(2),
            C_IN => C1,
            S => S(2),
            C_OUT => C2);
    adder3: adder
    port map(A => A(3),
            B => B(3),
            C_IN => C2,
            S => S(3),
            C_OUT => C_OUT)
end Behavioral;

```

Testbench

```

entity ripple_adder_tb is
-- Port ( );
end ripple_adder_tb;


architecture Behavioral of ripple_adder_tb is
component ripple_adder is
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      B : in STD_LOGIC_VECTOR (3 downto 0);
      C_IN : in STD_LOGIC;
      C_OUT : out STD_LOGIC;

```

```

        S : out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal A_TB, B_TB, S: STD_LOGIC_VECTOR(3 DOWNTO 0) := "0000";
signal C_IN, C_OUT : STD_LOGIC := '0';
begin
    ADDER:RIPPLE_ADDER
    PORT MAP(A => A_TB,
            B => B_TB,
            C_IN => C_IN,
            C_OUT => C_OUT,
            S => S);
    process
    begin
        wait for 5 ns;
        A_TB <= STD_LOGIC_VECTOR(UNSIGNED(A_TB) + 1);
        wait for 5 ns;
        B_TB <= STD_LOGIC_VECTOR(UNSIGNED(B_TB) + 1);
        wait for 5 ns;
        C_in <= not(C_IN);
    end process;
end Behavioral;

```

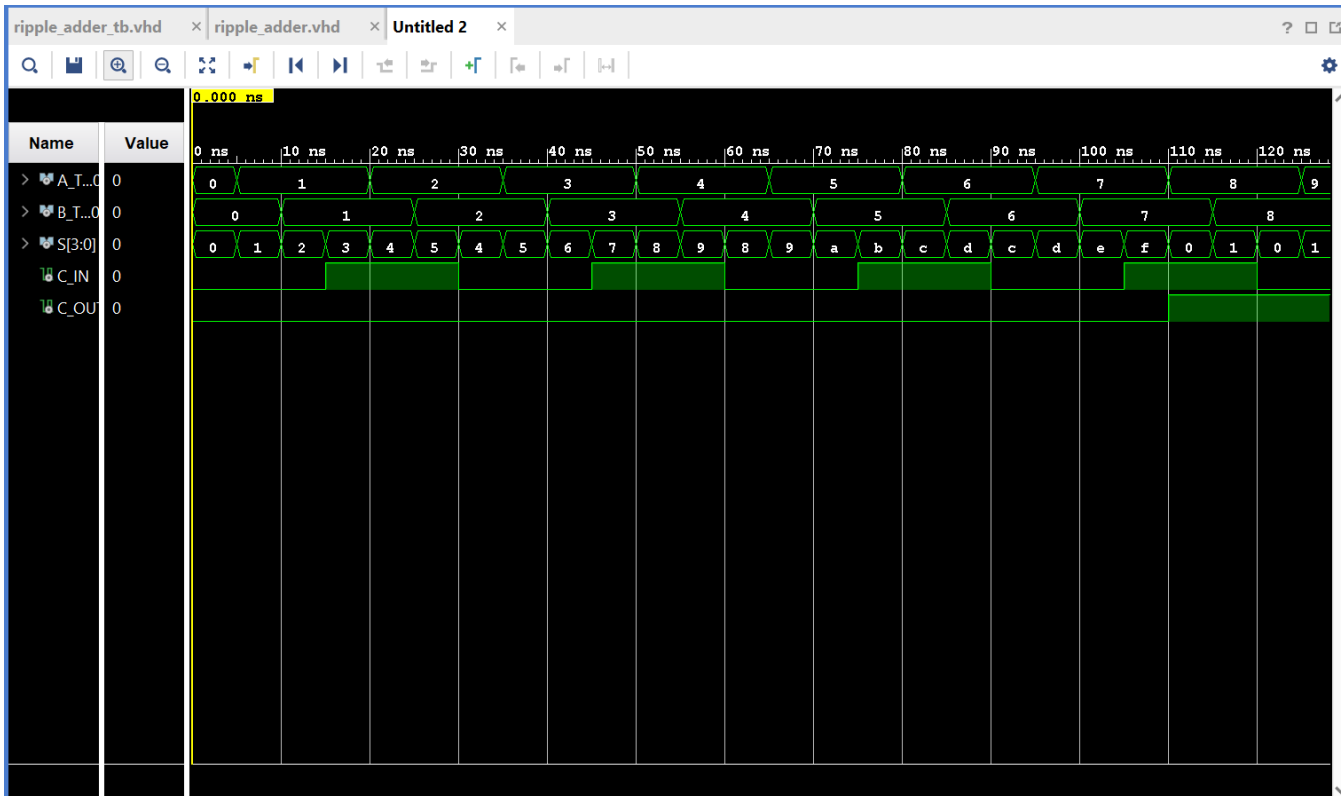


16 function 4 bit ALU

Operation

The circuit should take 3 four bit inputs (A, B, OP) and perform operations on A and B based on OP.

Schematic

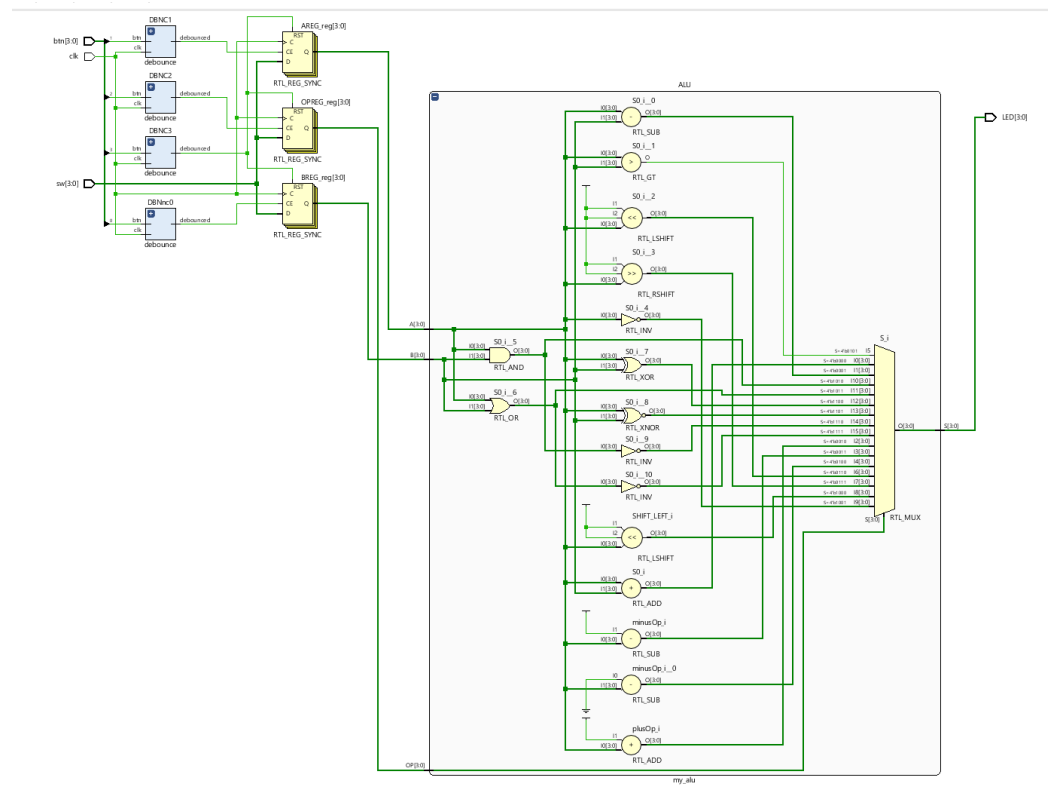

Design

entity my_alu is

Port (OP : in STD_LOGIC_VECTOR (3 downto 0);

A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

S : out STD_LOGIC_VECTOR (3 downto 0));

end my_alu;

architecture Behavioral of my_alu is

begin

process

begin

case OP is

when X"0" => S <= STD_LOGIC_VECTOR(UNSIGNED(A) + UNSIGNED(B));

when X"1" => S <= STD_LOGIC_VECTOR(UNSIGNED(A) - UNSIGNED(B));

when X"2" => S <= STD_LOGIC_VECTOR(UNSIGNED(A) + 1);

```

when X"3" => S <= STD_LOGIC_VECTOR(UNSIGNED(A) - 1);
when X"4" => S <= STD_LOGIC_VECTOR(0 - UNSIGNED(A));
when X"5" => S <= x"1" when (UNSIGNED(A) > UNSIGNED(B)) else x"0";
when X"6" => S <= STD_LOGIC_VECTOR(UNSIGNED(A) sll 1);
when X"7" => S <= STD_LOGIC_VECTOR(UNSIGNED(A) srl 1);
when X"8" => S <= STD_LOGIC_VECTOR(SHIFT_LEFT(UNSIGNED(A),1));
when X"9" => s <= NOT(A);
when X"A" => S <= A AND B;
when X"B" => S <= A OR B;
when X"C" => S <= A XOR B;
when X"D" => S <= A XNOR B;
when X"E" => S <= A NAND B;
when X"F" => S <= A NOR B;
end case;
end process;
end Behavioral;

```

Implementation

